



Learn Git and GitHub without any code!

Using the Hello World guide, you'll start a branch, write comments, and open a pull request.

[Read the guide](#)

[xrysav25](#) / [Digital-electronics-1](#)

[Code](#)

[Issues](#)

[Pull requests](#)

[Actions](#)

[Projects](#)

[Wiki](#)

[Security](#)

[Insights](#)

[Settings](#)

[main](#) ▾



[Digital-electronics-1](#) / [04-segment](#) / [README.md](#)



[xrysav25](#) Update README.md



1 contributor

[Raw](#)

[Blame](#)




175 lines (168 sloc) | 6.25 KB

Lab 4

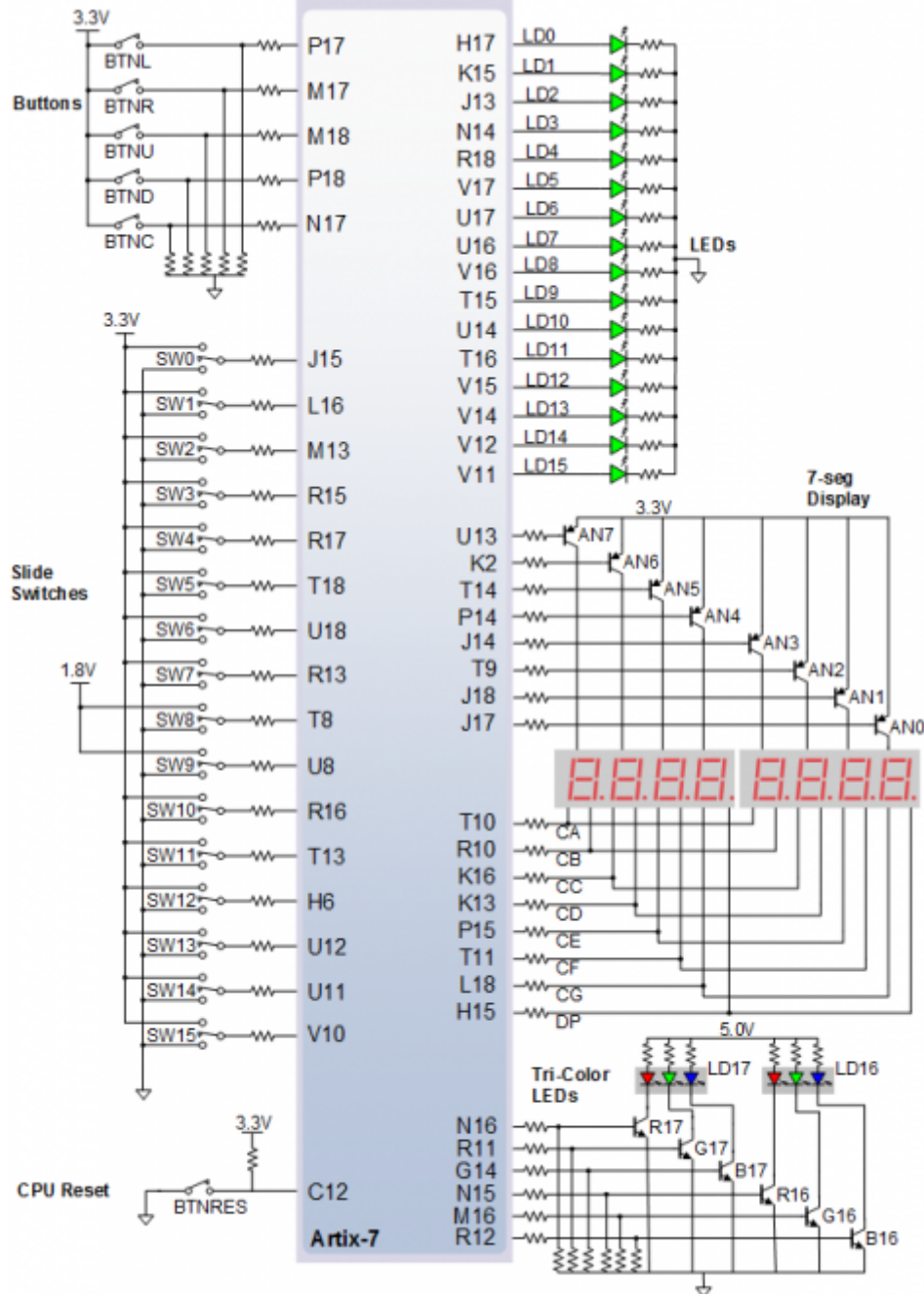1. Preparation tasks

- Figure or table with connection of 7-segment displays on Nexys A7 board



- Decoder truth table common anode

Hex	Inputs	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	1	0	1	1	0	0
5	0101	0	1	0	0	1	0	0

Hex	Inputs	A	B	C	D	E	F	G
6	0110	0	1	0	0	0	0	0
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
d	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0

2. Seven-segment display decoder

- architecture

```

p_7seg_decoder : process(hex_i)
begin
    case hex_i is
        when "0000" =>
            seg_o <= "0000001";    -- 0
        when "0001" =>
            seg_o <= "1001111";    -- 1
        when "0010" =>
            seg_o <= "0010010";    -- 2
        when "0011" =>
            seg_o <= "0000110";    -- 3
        when "0100" =>
            seg_o <= "1101100";    -- 4
        when "0101" =>
            seg_o <= "0100100";    -- 5
        when "0110" =>
            seg_o <= "0100000";    -- 6
        when "0111" =>
            seg_o <= "0001111";    -- 7
        when "1000" =>
            seg_o <= "0000000";    -- 8
        when "1001" =>
            seg_o <= "0000100";    -- 9
        when "1010" =>
            seg_o <= "0001000";    -- A
    end case;
end process;

```

```

    when "1011" =>
        seg_o <= "1100000";    -- B
    when "1100" =>
        seg_o <= "0110001";    -- C
    when "1101" =>
        seg_o <= "1000010";    -- D
    when "1110" =>
        seg_o <= "0110000";    -- E
    when others =>
        seg_o <= "0111000";    -- F
    end case;
end process p_7seg_decoder;

```

- stimulus

```

p_stimulus : process
begin
    s_hex <= "0000"; wait for 50ns;
    assert (s_seg = "0000001") report "Test failed for hex input combination: 000"
    s_hex <= "0001"; wait for 50 ns;
    assert (s_seg = "1001111") report "Test failed for hex input combination: 000"
    s_hex <= "0010"; wait for 50 ns;
    assert (s_seg = "0010010") report "Test failed for hex input combination: 001"
    s_hex <= "0011"; wait for 50 ns;
    assert (s_seg = "0000110") report "Test failed for hex input combination: 001"
    s_hex <= "0100"; wait for 50 ns;
    assert (s_seg = "1101100") report "Test failed for hex input combination: 010"
    s_hex <= "0101"; wait for 50 ns;
    assert (s_seg = "0100100") report "Test failed for hex input combination: 010"
    s_hex <= "0110"; wait for 50 ns;
    assert (s_seg = "0100000") report "Test failed for hex input combination: 011"
    s_hex <= "0111"; wait for 50 ns;
    assert (s_seg = "0001111") report "Test failed for hex input combination: 011"
    s_hex <= "1000"; wait for 50 ns;
    assert (s_seg = "0000000") report "Test failed for hex input combination: 100"
    s_hex <= "1001"; wait for 50 ns;
    assert (s_seg = "0000100") report "Test failed for hex input combination: 100"
    s_hex <= "1010"; wait for 50 ns;
    assert (s_seg = "0001000") report "Test failed for hex input combination: 101"
    s_hex <= "1011"; wait for 50 ns;
    assert (s_seg = "1100000") report "Test failed for hex input combination: 101"
    s_hex <= "1100"; wait for 50 ns;
    assert (s_seg = "0110001") report "Test failed for hex input combination: 110"
    s_hex <= "1101"; wait for 50 ns;
    assert (s_seg = "1000010") report "Test failed for hex input combination: 110"
    s_hex <= "1110"; wait for 50 ns;
    assert (s_seg = "0110000") report "Test failed for hex input combination: 111"
    s_hex <= "1111"; wait for 50 ns;
    assert (s_seg = "0111000") report "Test failed for hex input combination: 111"
end process p_stimulus;

```

• testbench



• top.vhd

architecture Behavioral of top is

begin

```
-----
-- Instance (copy) of hex_7seg entity
hex2seg : entity work.hex_7seg
  port map(
    hex_i      => SW,
    seg_o(6)   => CA,
    seg_o(5)   => CB,
    seg_o(4)   => CC,
    seg_o(3)   => CD,
    seg_o(2)   => CE,
    seg_o(1)   => CF,
    seg_o(0)   => CG
  );

-- Connect one common anode to 3.3V
AN <= b"1111_0111";

-- Display input value on LEDs
LED(3 downto 0) <= SW;
```

3. LED(7:4) indicators

• truth table

Hex	Inputs	LED4	LED5	LED6	LED7
0	0000	1	0	0	0
1	0001	0	0	1	1

Hex	Inputs	LED4	LED5	LED6	LED7
2	0010	0	0	0	1
3	0011	0	0	1	0
4	0100	0	0	0	1
5	0101	0	0	1	0
6	0110	0	0	0	0
7	0111	0	0	1	0
8	1000	0	0	0	1
9	1001	0	0	1	0
A	1010	0	1	0	0
b	1011	0	1	1	0
C	1100	0	1	0	0
d	1101	0	1	1	0
E	1110	0	1	0	0
F	1111	0	1	1	0

- code

```
-- LED(7:4) indicators
-- Turn LED(4) on if input value is equal to 0, ie "0000"
-- WRITE YOUR CODE HERE
LED(4) <= '1' when (SW= "0000") else '0';
-- Turn LED(5) on if input value is greater than "1001", ie 9
-- WRITE YOUR CODE HERE
LED(5) <= '1' when (SW= "1001") else '0';
-- Turn LED(6) on if input value is odd, ie 1, 3, 5, ...
-- WRITE YOUR CODE HERE
LED(6) <= '1' when (SW(0)= '1') else '0';
-- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
-- WRITE YOUR CODE HERE
LED(4) <= '1' when (SW = "0001") else
    '1' when (SW = "0010") else
    '1' when (SW = "0100") else
    '1' when (SW = "1000") else
    '0';
```

• testbench

